

# Lecture 5

## Basic Addition and Counting

### Half Adders and Full Adders


Basic building blocks for arithmetic circuits

#### Half Adder

Inputs:  $x, y$

Outputs:  $s = x \oplus y$

$$c = x \cdot y$$

 


#### Full Adder

Inputs:  $x, y, c_{in}$


Outputs:  $s = x \oplus y \oplus c_{in}$
 
$$c_{out} = x \cdot y + (x + y) \cdot c_{in}$$



Also called a  
(3,2) Counter

## Full Adder

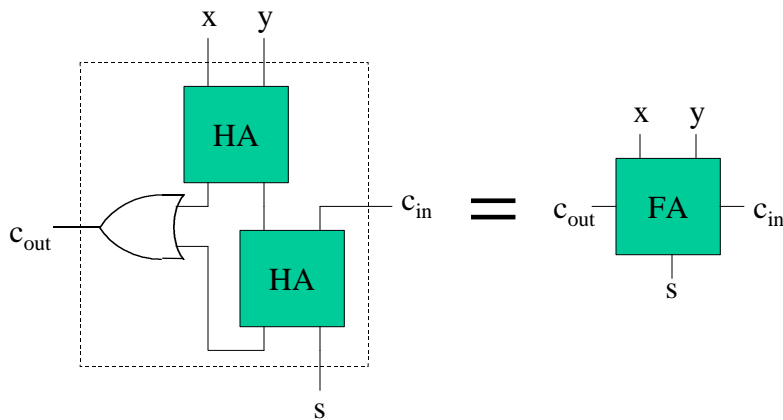

## Mixed Positive and Negative Binary Full Adders


+ Digit Set =  $\{0,1\}$     - Digit Set =  $\{-1,0\}$

+	
0	0
1	1


-	
-1	0
0	1

Excess-1  
encoding


Digit Encodings

 

## More Mixed Binary Full Adders

 

## Mixed Binary Additions

 

Propagate the digit sets.

You can add any combination of +/-  
to any other combination of +/-


## Converting Two's Comp to +/-

Two's complement number




Mixed +/- digit set number

## Half Adder

 


18 T


## Full adder

 

## CMOS Full Adder

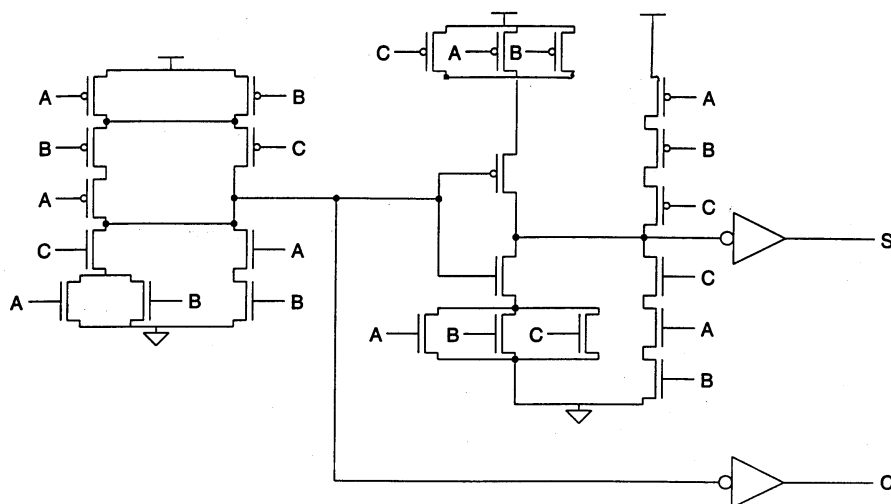


## Ripple Carry Adder

 

Worst case delay path

## Serial Addition

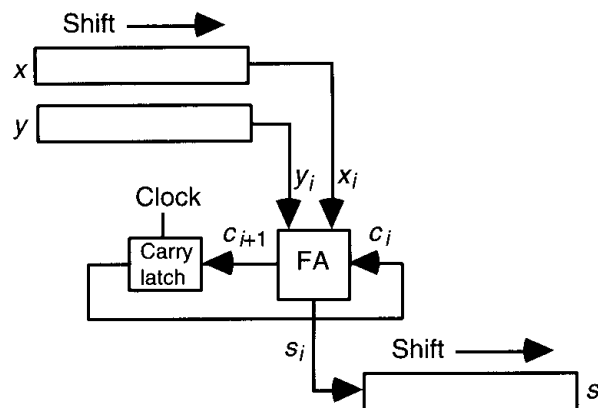

(a) Bit-serial adder.

## Conditions, Flags, and Exceptions

- Overflow - The output cannot be represented in the format of the result.
- Sign - 1 if the result is negative,  
0 if the result is positive.
- Zero - The result is zero.

## Signed Overflow

- $\text{Overflow}_{\text{two's-comp}} = \text{sign of result is wrong}$ 

$$= x_{k-1}y_{k-1}\bar{s}_{s-1} + \bar{x}_{k-1}\bar{y}_{k-1}s_{s-1}$$

when  $c_{k-1} = 1$

$$= \underbrace{x_{k-1}y_{k-1}\bar{s}_{s-1}}_0 + \underbrace{\bar{x}_{k-1}\bar{y}_{k-1}s_{s-1}}_{\bar{c}_k}$$

when  $c_{k-1} = 0$

$$= \underbrace{x_{k-1}y_{k-1}\bar{s}_{s-1}}_{c_k} + \underbrace{\bar{x}_{k-1}\bar{y}_{k-1}s_{s-1}}_0$$

$$= c_k \cdot \bar{c}_{k-1} + \bar{c}_k \cdot c_{k-1}$$

$$= c_k \oplus c_{k-1}$$

## Unsigned Overflow

- $\text{Overflow}_{\text{unsigned}} = \text{carry out of last stage}$   
 $= c_k$

## Sign

$\text{Sign}_{\text{signed}} = 0$  when positive, 1 when negative

$$= s_{k-1} \quad \text{when Overflow} = 0$$

$$= \bar{s}_{k-1} \quad \text{when Overflow} = 1$$

$$= s_{k-1} \oplus \text{Overflow}$$

$$= s_{k-1} \oplus c_k \oplus c_{k-1}$$


$\text{Sign}_{\text{unsigned}} = 0$  (always positive!)




## Zero

$$\text{Zero} = \bar{s}_{k-1} \cdot \bar{s}_{k-2} \cdot \dots \cdot \bar{s}_0 \quad (\text{both signed, unsigned})$$

$k$  - input NOR gate

 

## Adder with Flag Detection

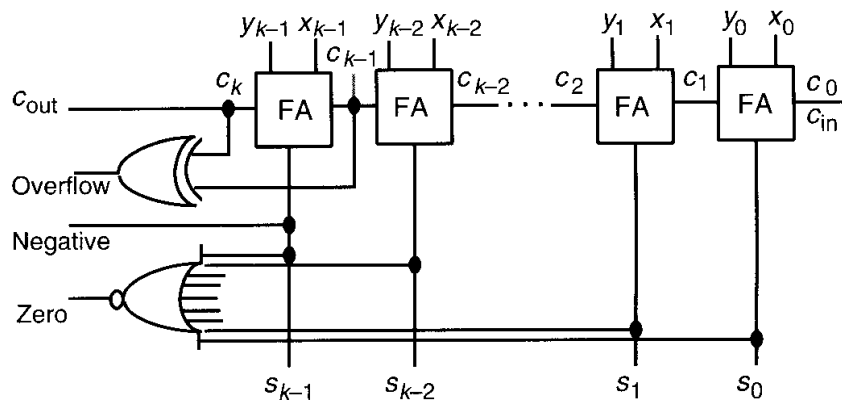


What's wrong with the diagram from the book ?

## Flag Summary

<i>Flag</i>	<i>Sign</i>	<i>Unsigned</i>
<i>Overflow</i>	$c_k \oplus c_{k-1}$	$c_k$
<i>Sign</i>	$c_k \oplus c_{k-1} \oplus s_{k-1}$	0
<i>Zero</i>	$\bar{s}_{k-1} \cdot \bar{s}_{k-2} \cdots \bar{s}_0$	$\bar{s}_{k-1} \cdot \bar{s}_{k-2} \cdots \bar{s}_0$

## Analysis of Carry Propagation

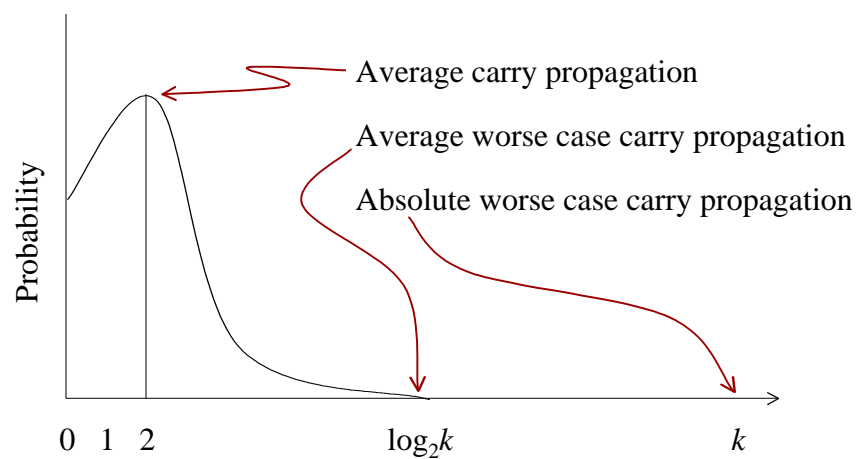


Asynchronous circuits must wait average worst case,  
synchronous circuits must wait absolute worst case

## Carry Completion Detection

- For asynchronous arithmetic, (not useful for synchronous arithmetic)
- Carry Completion Detection gives a *done* signal when carry chain is done.
- Average time  $\propto \log_2 k$
- Two rail logic:

$b_i \ c_i$	
0 0	Carry not known yet
0 1	Carry known to be 1
1 0	Carry known to be 0

## Carry Completion Detection

 

## Speeding Up Addition

### Making Low Latency Carry Chains

- From point of view of carry propagation
  - computation of *sum* is not important.
  - At each position a carry is either
    - generated :  $x_i + y_i \geq r$
    - propagated :  $x_i + y_i = r - 1$ , or
    - annihilated :  $x_i + y_i < r - 1$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i \oplus y_i)}_{p_i} \cdot c_i$$

$$\begin{aligned} c_{i+1} &= g_i + p_i \cdot c_i \\ s_i &= p_i \oplus c_i \end{aligned}$$

“Carry  
Recurrence”


## Propagation of Carry

$$\begin{aligned} c_{i+1} &= g_i + p_i c_i \\ &= g_i (1 + c_i) + p_i c_i \\ &= g_i + \underbrace{(g_i + p_i)}_{t_i} \cdot c_i \\ &= g_i + t_i c_i \\ t_i &= x_i + y_i \end{aligned}$$


## Propagation of Inverse Carry

$$\begin{aligned}
 \bar{c}_{i+1} &= \overline{g_i + p_i c_i} \\
 &= \bar{g}_i \cdot (\bar{p}_i + \bar{c}_i) \\
 &= \bar{g}_i \bar{p}_i + \bar{g}_i \bar{c}_i \\
 &= a_i + (a_i + p_i) \cdot \bar{c}_i \\
 &= a_i + p_i \bar{c}_i
 \end{aligned}$$

## Manchester Carry Chains

 

**(a)** Conceptual representation.

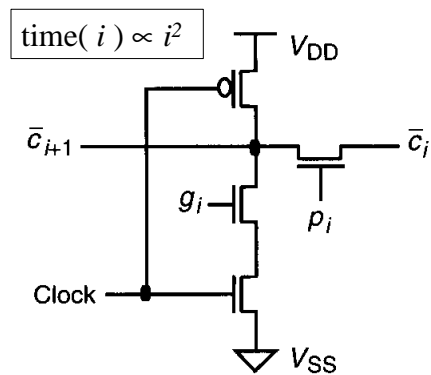

**(b)** Possible CMOS realization.