Lecture 8 Multioperand Addition

Uses of Multioperand Addition


- Multiplication
 - partial products are formed and must be added
- Inner-product computation (Dot Product, Convolution, FIR filter, IIR filter, etc.)
 - terms must be added

^ • • • •	X
••••	x ₀ a2 ⁰ x ₁ a2 ¹ x ₂ a2 ² x ₃ a2 ³
•••••	p
•••••	p(0) p(1) p(2) p(3) p(4) p(5) p(6)
•••••	s

"Dot Notation"

- Useful when positioning or alignment of the bits, rather that there values, is important.
 - Each dot represents a digit in a positional number system.
 - Dots in the same column have the same positional weight.
 - Rightmost column is the least significant position.


Serial Multioperand Addition

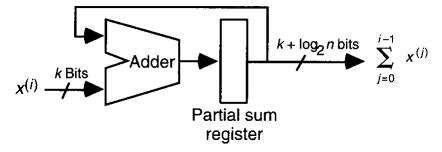


Operands $x^{(0)}$, $x^{(1)}$, ..., $x^{(n-1)}$ are shifted in, one per clock cycle.


Final sum can be as large as $n(2^k - 1)$.

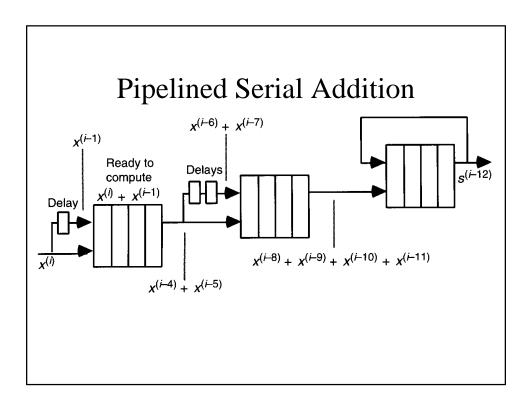Partial sum register must be $\log_2(n2^k-n+1) \approx k + \log_2 n$ bits wide.



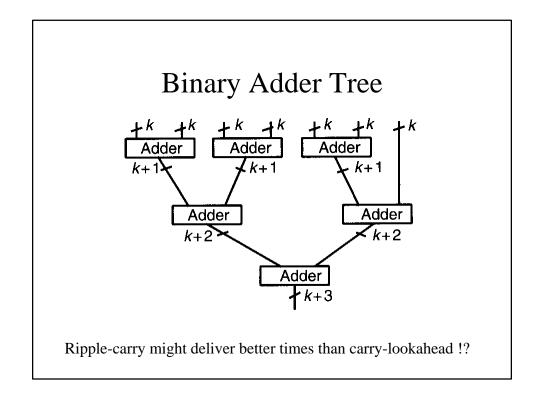

Analysis of Ripple-Carry Tree Adder

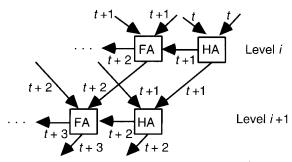

$$T_{\text{tree-ripple-multi-add}} = O(k + \log n)$$

Whereas, for carry-lookahead adders

$$T_{\text{tree-fast-multi-add}} = O(\log k + \log(k+1) + \dots + \log(k + \lceil \log_2 n \rceil - 1))$$


= $O(\log n \log k + \log n \log \log n)$


Can we do better?


$$T_{\text{tree-ripple-multi-add}} = O(k + \log n)$$


The absolute minimum time is $O(\log(kn)) = O(\log k + \log n)$, where kn is the total number of input bits.

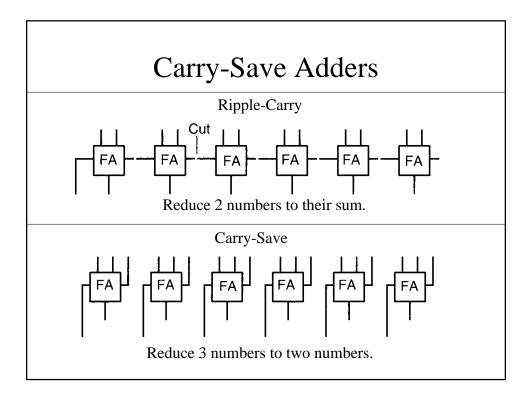
The minimum is achievable with (next slide please)



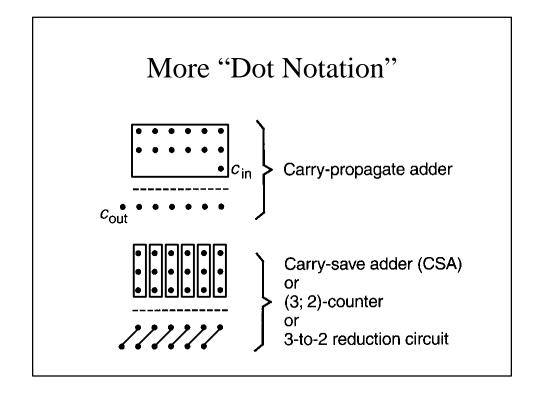

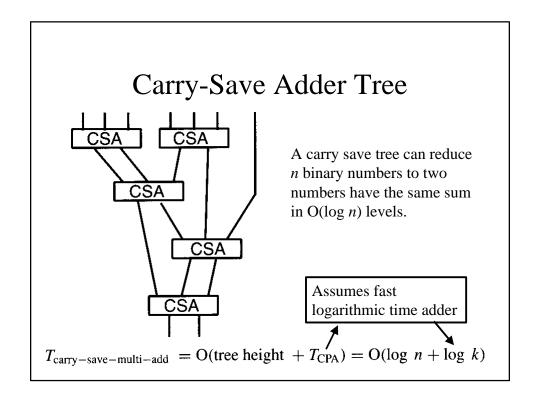

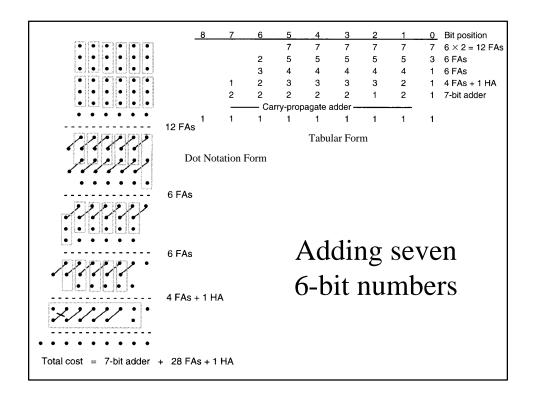

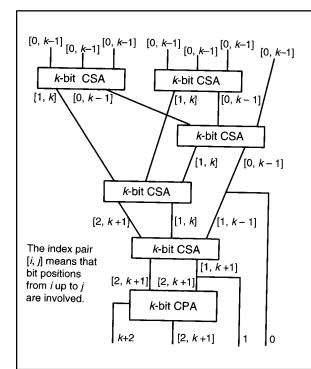

Seven Input Wallace Tree

In general, an n-input Wallace tree reduces its k-bit inputs to two $(k + \log_2 n - 1)$ -bit outputs.

Analysis of Wallace Trees

• The smallest height h(n) of an n-input Wallace tree, satisfies the recurrence:

$$h(n) = 1 + h([2n/3])$$

solution: $h(n) \ge \log_{1.5}(n/2)$

• The number of inputs n(h) that can be reduced to two outputs by an h-level tree, satisfies the recurrence:

$$n(h) = \lfloor 3n(h-1)/2 \rfloor$$

solution: upper bound: $n(h) \le 2(3/2)^h$.

lower bound: $n(h) > 2(3/2)^{h-1}$

Max number of inputs n(h) for an h-level tree


h	n(h)	h	n(h)	h	n(h)
0	2.	7	28	14	474
1	3	8	42	15	711
2	4	9	63	16	1066
3	6	10	94	17	1599
1	q	11	141	18	2398
5	13	12	211	19	3597
6	19	13	316	20	5395


Wallace Tree

- Reduce the number of operands at the earliest opportunity.
- If there are m dots in a column, apply $\lfloor m/3 \rfloor$ full adders to that column.
- Tends to minimize overall delay by making the final CPA as short as possible.

Dadda Trees

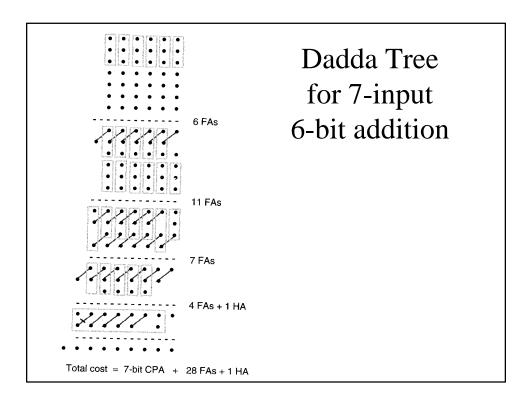
- Reduce the number of operands in the tree to the next lower n(h) number in the table using the fewest FA's and HA's possible.
- Reduces the hardware cost without increasing the number of levels in the tree.




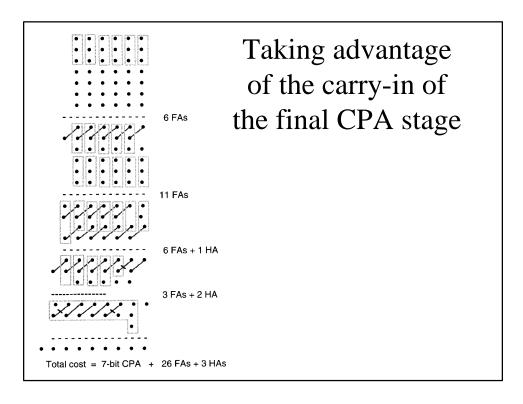

Parallel Counters

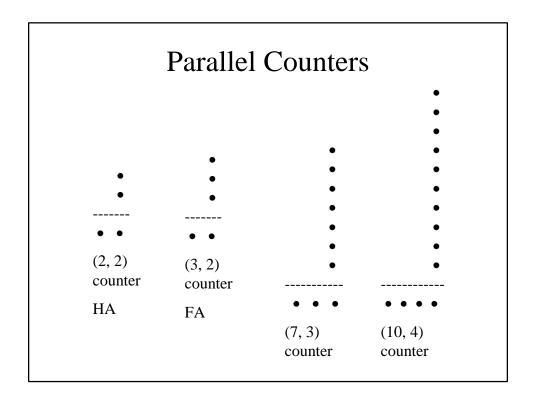
- Receives *n* inputs
- Counts the number of 1's among the *n* inputs
- Outputs a $\lfloor \log_2(n+1) \rfloor$ bit number
- Reduces n dots in the same bit position to $\lfloor \log_2(n+1) \rfloor$ dots in different positions.



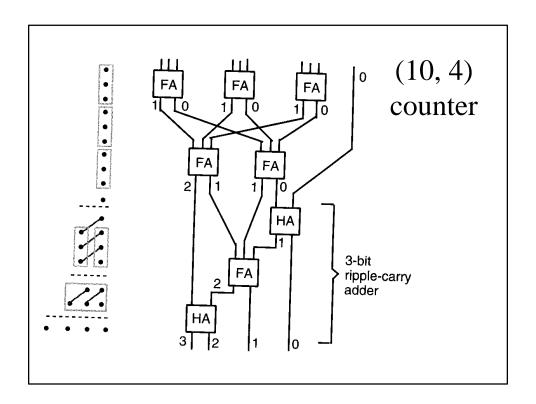


Generalized Parallel Adders

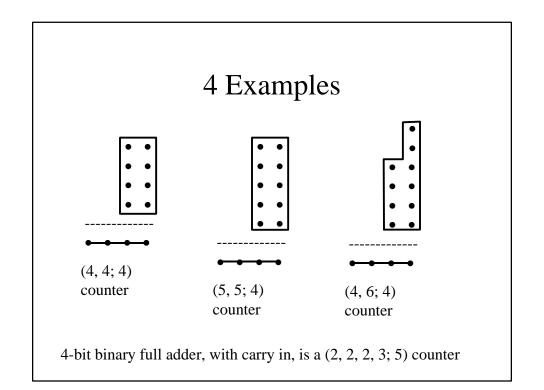- Reduces "dot patterns" (not necessarily in the same column) to other dot patterns (not necessarily only one in the each column).
- Book speaks less generally, and restricts output to only one dot in each column.




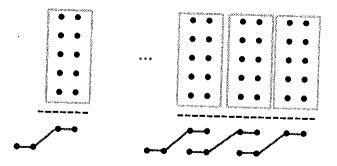Reducing 5 Numbers with (5, 5; 4) Counters



(n; 2) Counters

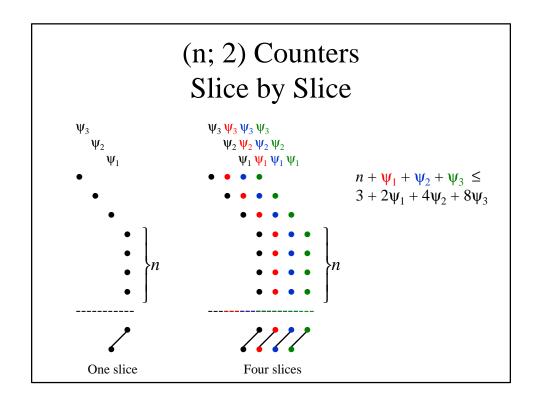- Difference in notation from other counters.
- Reduce *n* (larger than 3) numbers to two numbers.
- Each slice *i* of an (*n*; 2) counter:
 - receives carry bits from one or more positions to the right (*i*-1, *i*-2,)
 - produces outputs to positions i and i+1
 - produces carries to one or more positions to the left (i+1, i+2,)



Adding Multiple Signed Numbers

• By means of sign extension

Extended positions	Sign	Magnitude positions
$x_{k-1} x_{k-1} x_{k-1} x_{k-1} x_{k-1}$	x_{k-1}	$x_{k-2} x_{k-3} x_{k-4} \cdots$
y_{k-1} y_{k-1} y_{k-1} y_{k-1} y_{k-1}	y_{k-1}	$y_{k-2} y_{k-3} y_{k-4} \cdots$
z_{k-1} z_{k-1} z_{k-1} z_{k-1} z_{k-1}	z_{k-1}	$z_{k-2} z_{k-3} z_{k-4} \cdots$

• By method of negative weighted sign bits

Extended positions 1 1 1 1 0
$$\overline{x}_{k-1}$$
 Magnitude positions $x_{k-2} x_{k-3} x_{k-4} \cdots \overline{y}_{k-1}$ $y_{k-2} y_{k-3} y_{k-4} \cdots \overline{z}_{k-1}$ $z_{k-2} z_{k-3} z_{k-4} \cdots \overline{z}_{k-1}$